

ADAM v32: Power Connection & Management Guide

A stable robot requires clean, isolated power. If the servos share power directly through the Raspberry Pi or ESP32-CAM pins, the motors will cause voltage spikes (brownouts) that will crash the AI, drop the Wi-Fi, or cause the audio to stutter.

This guide outlines a **Central 5V Rail** architecture to safely power the Body and Head components.

1. The Power Source & The Golden Rule

- **The Battery:** A standard 2S LiPo (7.4V) or 18650 battery pack.
- **The Buck Converter:** You must use a **5V Step-Down Buck Converter** rated for at least **3 Amps** (e.g., LM2596 or MP1584).
- **THE GOLDEN RULE:** **All grounds must be connected together.** The Pi, ESP32-CAM, Pico, Amplifier, Servos, and Buck Converter **MUST** share a common Ground (GND). If they don't, I2S audio and UART serial communication will fail.

2. Body Power Distribution (The Base)

The 5V output from the Buck Converter creates your **Main 5V Rail**.

Component	Power Pin	Connects To	Voltage Required	Notes
Raspberry Pi Zero 2W	5V (Pin 2 or 4)	Main 5V Rail	5V	Powers the brain.
MAX98357A (Amp)	VIN	Main 5V Rail	5V	Needs high current for the 3W speaker.
MG90S Pan Servo	VCC (Red Wire)	Main 5V Rail	5V	NEVER power from Pi. Connect directly to rail.
RCWL-0516 Radar	VIN	Main 5V Rail	5V	Contains its own internal 3.3V regulator.

INMP441 Mics (x2)	VDD	Pi 3.3V (Pin 1 or 17)	3.3V	 CRITICAL: Mics must use 3.3V from the Pi. Using 5V will fry the Pi's I2S data pins.
-------------------	-----	-----------------------	------	--



3. The Neck Joint (Power Passthrough)

To power the head, run two appropriately thick wires (e.g., 22 AWG) from the **Main 5V Rail** in the body, straight up through the mechanical neck, into the head.

1. **Head 5V Wire**
2. **Head GND Wire**

(If using Flow 2 "Full Hardwired" from the Blueprint, you will also pass the Pi TX and Pi RX wires here).



4. Head Power Distribution (The Moving Part)

Inside the head, split the 5V and GND wires you passed through the neck to create a **Head 5V Rail**.

Component	Power Pin	Connects To	Voltage Required	Notes
ESP32-CAM	5V Input	Head 5V Rail	5V	The ESP32-CAM has a built-in 3.3V regulator for its logic.
Raspberry Pi Pico	VSYS (Pin 39)	Head 5V Rail	5V	Do not use VBUS if powering via battery. VSYS is safest.
MG90S Tilt Servo	VCC (Red Wire)	Head 5V Rail	5V	NEVER power from ESP/Pico. Connect directly to rail.

ILI9341 TFT Display	VCC & LED	Pico 3V3(OUT) Pin 36	3.3V	 CRITICAL: Feeding 5V to the TFT logic can fry it. Use the Pico's clean 3.3V output.
PCF8574T Expander	VCC	ESP32-CAM 3.3V Pin	3.3V	Keeps I2C logic levels strictly at 3.3V.
TTP223 Touch (x4)	VCC	ESP32-CAM 3.3V Pin	3.3V	Draws very little current. Daisy-chain from the expander's power.



5. Final Safety Checklist

1. **Servo Isolation:** Check the red wires for both MG90S servos. They must trace back directly to the Buck Converter's 5V output, **not** to a pin on the Raspberry Pi or ESP32-CAM.
2. **Audio Logic Safety:** Check the VDD pins on both INMP441 microphones. They must go to the Raspberry Pi's 3.3V pin.
3. **Display Logic Safety:** Check the VCC and LED pins on the TFT Display. They must go to the Raspberry Pi Pico's 3.3V pin.
4. **Common Ground:** Use a multimeter in continuity mode. Touch the metal shielding of the Pi's USB port, the metal shielding of the ESP32-CAM's SD slot, and the GND pin of the Amplifier. They should all beep (showing they share the same ground).